


## 15ECE202 Digital Circuits and Systems

(Common to Computer Science and Engineering, Electronics and Communication Engineering and  
Electronics and Instrumentation Engineering)

Time: Two hours      Maximum: 50 Marks

### Answer all questions

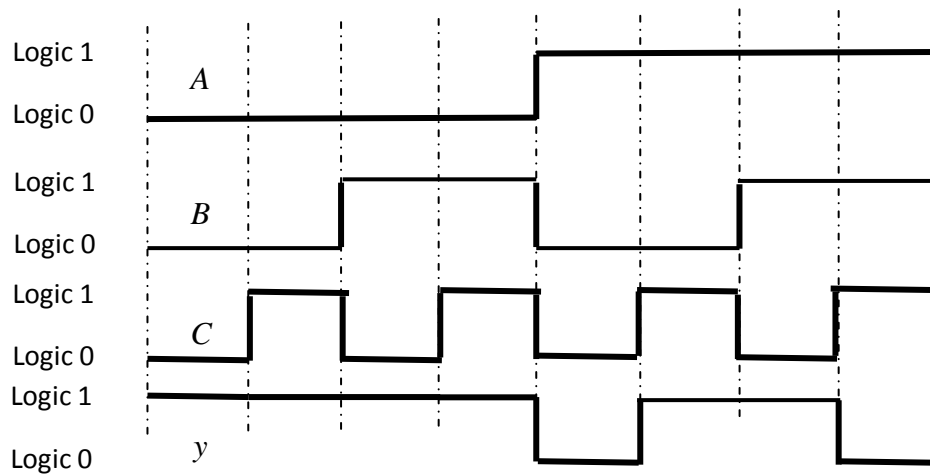1. (a) Express the decimal number 123 in hexadecimal form. (2)  
(b) Determine the base of the system where the sum  $23 + 56 = 112$  is valid. (4)  
(c) Simplify the expression  $F = \bar{A}BCD + \bar{A}\bar{C}D + B\bar{C}D + \bar{A}\bar{C}\bar{D} + \bar{A}B\bar{C}D$  without using K-map (4)
2. (a) Data from a sensor is encoded in three bits  $b_2b_1b_0$ . When this three bit value exceeds 4, an alarm output  $al$  has to be asserted to logic 1. Write the truth table for the circuit and derive minimized Boolean expression for  $al$  using only Boolean identities (without using K-map) (3)  
(b) Using Boolean identities convert the given SoP expression into canonical form  
 $F(A, B, C, D) = \bar{A} + B + CD$  (3)  
(c) Determine the maxterms of the following PoS expression  
 $F(A, B, C, D) = (\bar{A} + B + C)(C + \bar{D})$  (4)
3. A digital circuit has 3 inputs  $A$ ,  $B$  and  $C$ . The waveforms shown below are applied to the inputs. The response in the output  $y$  is also plotted. Derive a minimized Boolean SoP expression for  $y$  using a K-Map. Implement using only NAND gates (10)



4. Obtain a minimized Boolean expression for the following truth table using tabulation method **(10)**

$$F(A, B, C, D, E) = \sum m(3,5,7,9,11,15,17,19,21,23,25,27,29,31)$$

5. (a) Illustrate overflow with an example **(3)**

(b) Represent the following numbers in 2s complement signed form (i)  $-146$  (ii)  $+223$  (iii)  $-277$  (iv)  $+332$  **(4)**

(b) What is the word length of a twos complement adder/subtractor that can handle operands in the range  $-150$  to  $+150$  **(3)**

\* \* \* \* \*