

Roll No.: _____

Amrita VishwaVidyapeetham

B.Tech. Second Assessment – Oct/Nov. 2016

Third Semester

15ECE202 Digital Circuits and Systems

(Common to Computer Science and Engineering,
Electronics and Communication Engineering and Electrical and Electronics Engineering)

Time: Two hours

Maximum: 50 Marks

Answer all questions


1. (a) Implement the following truth table using a *single* MUX of appropriate size

$$F(A, B, C, D, E) = \sum m(0, 1, 5, 11, 16, 19, 21, 23, 29, 31)$$

(6 Marks)

- (b) Write the Boolean equation of the Boolean function F implemented by the following multiplexercircuit.

(4 Marks)

 

2. (a) Implement a full adder circuit using a single decoder and additional gates **(6 Marks)**
- (b) You are given a *4 to 2 priority encoder* and a *4:1 MUX*. There are four data lines coming from the following personnel in an office (mentioned in decreasing order of privilege) (i) *Manager* (ii) *Supervisor* (iii) *Operator* (iv) *Intern*. Show a block diagram describing how the given building blocks can be connected to provide privilege based access to a single outgoing data line for data from all the above sources. **(4 Marks)**
3. (a) Draw the circuit of a comparator for comparing two 3-bit binary numbers $A_2A_1A_0$ and $B_2B_1B_0$ having separate outputs for *greater than*, *less than* and *equal to* conditions. **(6 Marks)**
- (b) A 3-bit data is received from a sensor. If it exceeds 6 a letter “H” has to be displayed. If it falls below 3, a letter “L” has to be displayed. Draw a block diagram depicting how this can be accomplished using two 3-bit comparators, Multiplexers and a seven segment display. **(4 Marks)**
4. (a) Draw the circuit of an SR Latch using only NAND gates. Explain why the input combination $S = R = 1$ is undesirable **(4 Marks)**


(b) A flip-flop having two inputs A and B has the truth table (characteristic table) given below. Design the flip-flop using a D Flip-flop and additional gates as building blocks.

A	B	Q(t+1)
0	0	1
0	1	Q(t)
1	0	$\overline{Q(t)}$
1	1	0

(6 Marks)

5. (a) Draw the circuit of a 3-bit synchronous Up counter using D flip-flops and additional gates **(4 Marks)**

 (b) Determine the sequence generated by Q_1Q_0 in the following circuit when a continuous clock signal is applied to the CLK line. Assume that both flip-flops are initially preset to $Q_1 = Q_0 = 1$ **(6 Marks)**



* * * * *